

Circuit Analysis of the Matchless DC-30 Pentode Preamp



Ampbooks


Site: **30 Pentode Preamp**

Saved  Today at 20:57

...

"As used in the DC-30 - and the Vox AC15 (and briefly, the early AC30) that inspired it - an EF86 pentode preamp tube helps to create a sound in the amp's second channel that is really quite different from the classic Top Boost chime and shimmer most consider the 'classic Vox sound.' This tube yields a thick, rich tone with a full and relatively even reproduction of the frequency spectrum (as relates to the electric guitar)..." 1

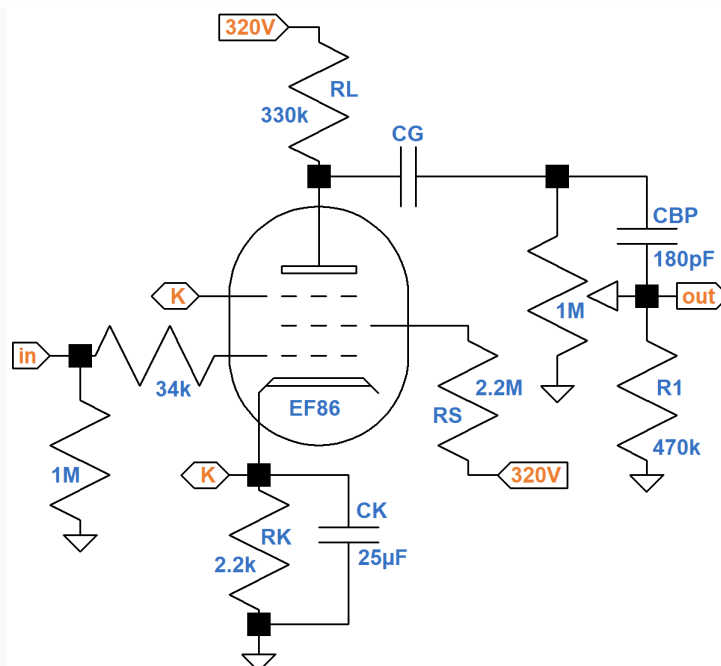The first stage for Channel 2 of the Matchless DC-30 guitar amplifier contains an EF86 pentode that drives the effects send or the phase inverter via a switchable coupling capacitor CG and a 1M Ω volume control.



CG is switched in 6 steps between 330pF (maximum bass cut) and 0.01 μ F (minimum bass cut).

The AC load varies from $1\text{M}\Omega \parallel 470\text{k}\Omega = 320\text{k}\Omega$ (volume at maximum) and $1\text{M}\Omega$ (volume near minimum, low frequencies, for which CBP acts as an open circuit). Because the plate resistance of a pentode is very high, the output impedance of a pentode voltage amplifier is approximately equal to the plate load resistor value R_L . By setting R_L equal to $330\text{k}\Omega$, Matchless creates an output impedance that approximately matches the lower limit of the AC load.


DC Operating Point

According to Ohm's Law, if the voltage across the $2.2\text{k}\Omega$ cathode resistor is 4V , then the cathode current is

$$4\text{V} / 2.2\text{k}\Omega = 1.82\text{mA}$$

This represents plate current plus screen current. According to the data sheet, the ratio of plate current to screen current is typically 5, so the plate current is $5/6$ of this value: 1.52mA .

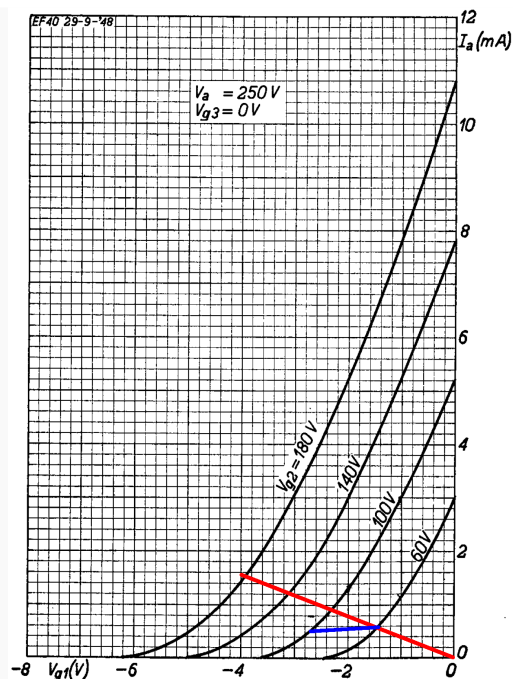If the voltage across the cathode resistor is zero, the plate current is zero. The endpoints for the red line shown here on the EF86 plate transfer characteristics are -4V , 1.52mA and 0V , 0mA .




If the screen voltage is 100V, the voltage drop across the $2.2\text{M}\Omega$ screen resistor is $320\text{V} - 100\text{V} = 220\text{V}$. According to Ohm's Law, the screen current through the resistor is 0.1mA , so the plate current is 5 times greater: 0.5mA . Repeating this logic for a 60V screen, the plate current is 0.59mA . These are the endpoints of the blue line. The lines intersect at a 60V screen.

According to the transfer characteristics, the DC grid bias is -1.4V . The DC plate current is 0.59mA , so the voltage drop across the $330\text{k}\Omega$ plate load resistor is

$$(0.59\text{mA})(330\text{k}\Omega) = 195\text{V}$$

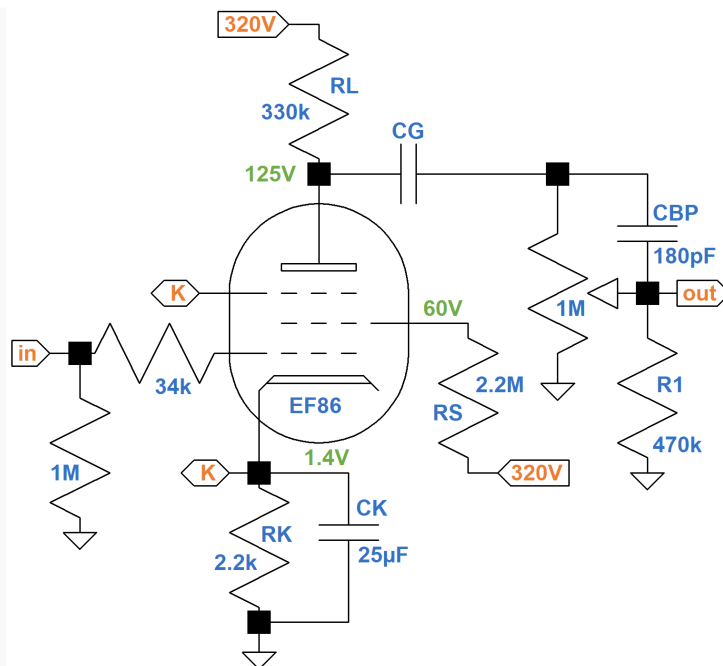The plate voltage is therefore $320\text{V} - 195\text{V} = 125\text{V}$. Here are our estimates of the DC voltages based on an average tube.




Voltage Gain


Based on the data sheet's typical transconductance of $g_m = 2\text{mS}$ (" $S = 2\text{ma/V}$ "), unloaded voltage gain is $g_m R_L = (2\text{mS})(330\text{k}\Omega) = 660$ (56dB), which is impressive - try getting that from a triode! The output impedance is approximately $330\text{k}\Omega$, however, so when the AC load is $320\text{k}\Omega$, voltage gain is reduced by a factor of $320\text{k}\Omega / (320\text{k}\Omega + 330\text{k}\Omega) = 0.49$ (-6.2dB). Gain is still much greater than for a typical 12AX7 stage.

Switched Tone Control

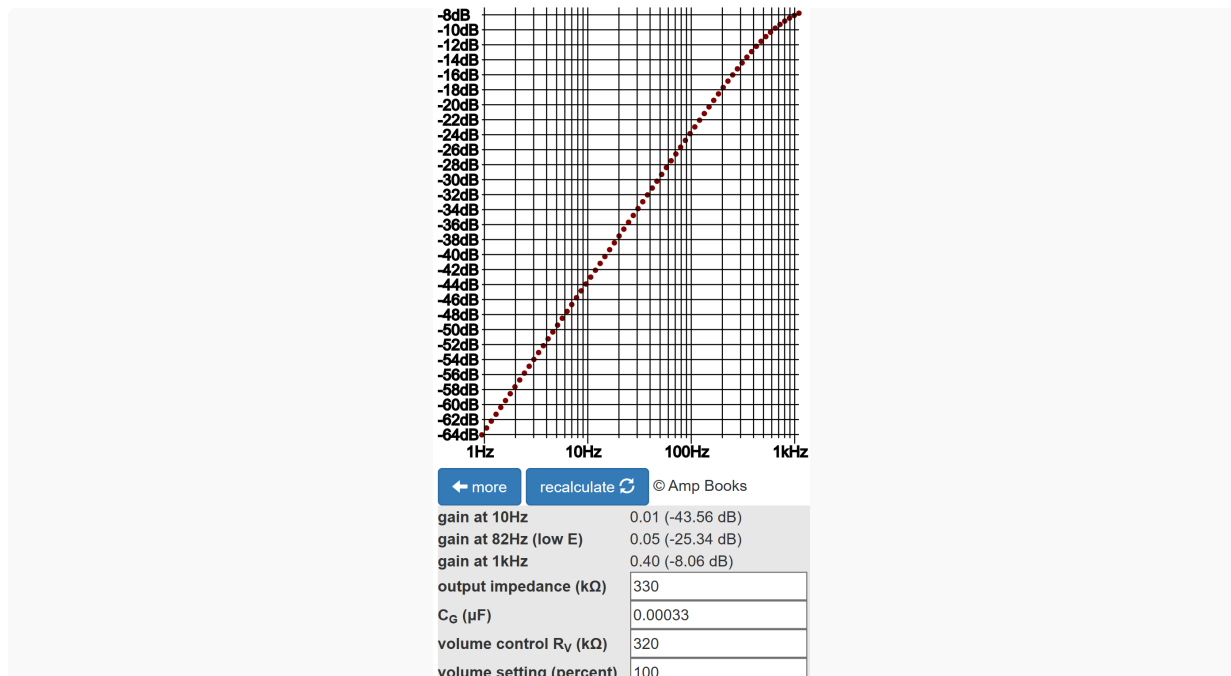Depending on switch position, CG takes on these values: 330pF , 560pF , $0.0012\mu\text{F}$, $0.0022\mu\text{F}$, $0.0047\mu\text{F}$, and $0.01\mu\text{F}$. According to the [Coupling Capacitor calculator](#), bass attenuation is most severe with the volume control at maximum ($320\text{k}\Omega$ AC load) and CG = 330pF . In fact, there is 8dB attenuation at 1kHz .



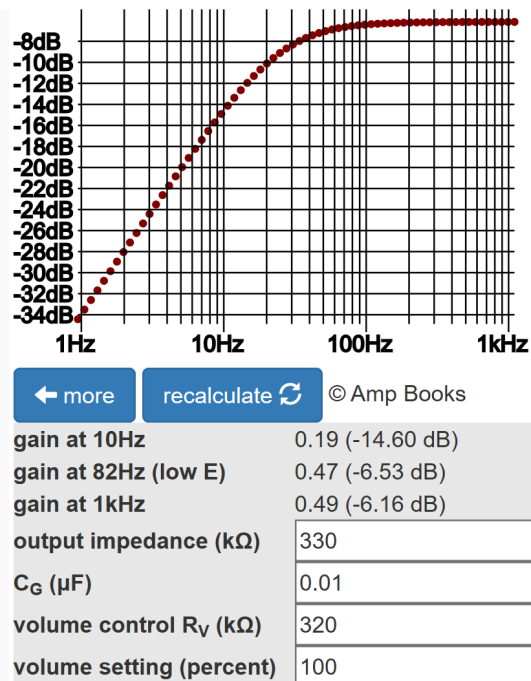With the knob fully clockwise, the coupling capacitor value is $0.01\mu\text{F}$ and there is only 0.4dB attenuation at 82Hz compared to 1kHz.



Reference

1Dave Hunter, **Amped**, (London: Voyageur Press, 2012), p. 199.