

Gustav Robert Kirchhoff's Current Law




Ampbooks

Site: **Ampbooks**

Saved  Today at 21:03

...

A node is a point in the circuit where components are connected together. We can think of the precise point as the solder connection, but the node actually includes all the wires and component leads connected to that point, because they are all at the same voltage. (This assumes that wires are perfect conductors, which is a reasonable assumption in most situations.) Consider, for example, the Ampeg B-22-X high-gain input circuit.

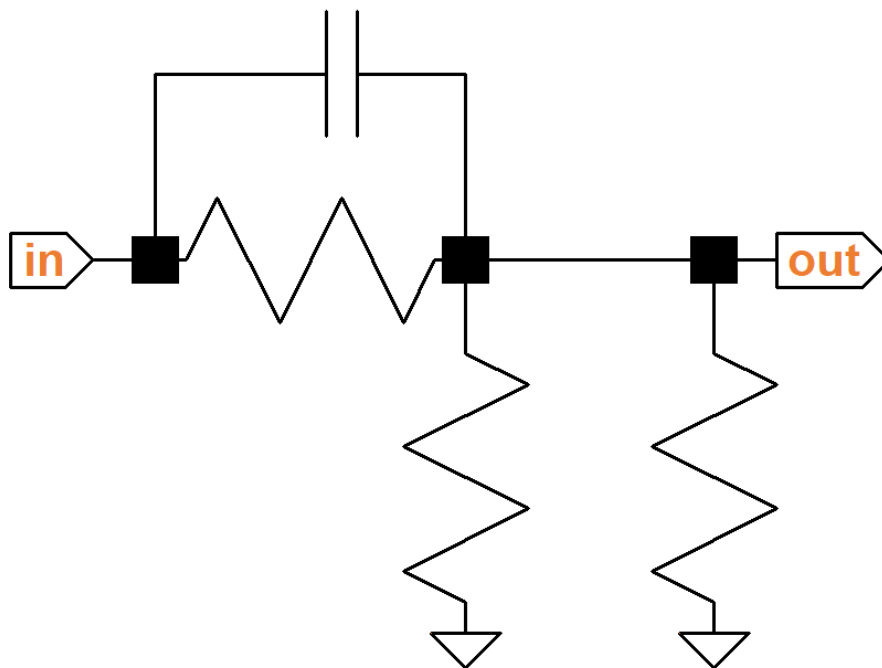

There are three nodes in this circuit: in, out, and ground.

Kirchhoff's Current Law

According to Kirchhoff's Current Law, or KCL as it is known, the sum of the currents entering a node equals the sum of the currents leaving a node.

Problem

Consider the screen supply of the Fender Bassman 5F6-A. At idle, the total current load of the power tube screens, the phase inverter, and the preamps is 11mA. This current is supplied via the choke, which smoothes out ripples in the flow. Suddenly we hit our power chord and bring the amp instantly to full power, where the screen current increases substantially, raising the total current load from 11mA to 27mA. After a few tenths of a second the current through the choke rises to 27mA, but initially all of the extra current is supplied by the capacitor. What is this initial current IC?

11mA 27mA IC

Solution

The unknown current IC and 11mA are entering the node in the upper right and 27mA is leaving it. According to Kirchhoff's Current Law

$$IC + 11mA = 27mA$$

Thus

$$IC = 16mA$$

KCL in Practice

Kirchhoff's Current Law allows us to determine an unknown current based on known currents. To be honest, his voltage law is more important to tube amps. The nuances of power supply sag and some power tube calculations are notable exceptions.